

12 DC Circuits – Resistors and Batteries

- “Zeroth Law:” Two points connected by an (ideal) wire are at the same potential.
- **Kirchoff’s First Law (junction rule / conservation of charge):** At any junction in an electric circuit, the total current entering the junction must be equal to the total current leaving the junction,


$$\sum_{\text{junction}} I_{in} = \sum_{\text{junction}} I_{out}$$

- **Kirchoff’s Second Law (loop rule / conservation of energy):** The algebraic (signed) sum of all differences in potential around a complete circuit loop must be zero.


$$\sum_{\text{loop}} \Delta V = 0$$

- Resistors in series add directly: $R_{eq} = \sum_i R_i$
- Resistors in parallel add as reciprocals (conductances $G = R^{-1}$ add directly): $R_{eq}^{-1} = \sum_i R_i^{-1}$
- Ohm’s law: $V = IR$, Power dissipated by a resistor: $P = IV = I^2R = V^2/R$

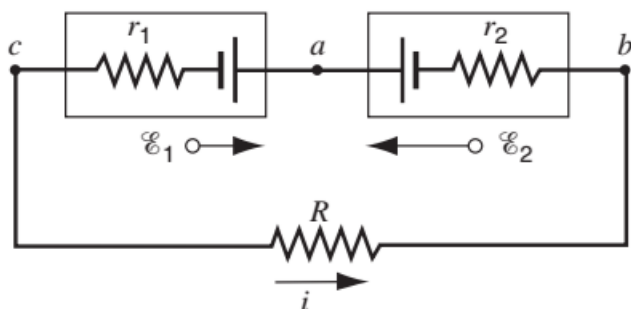
1. (RHK Sample 31-1+2) (a) What is the current i in the circuit shown below? (Given $\mathcal{E}_1, \mathcal{E}_2, r_1, r_2, R$)
 (b) What is the potential difference between points a and b ? (c) What is the potential difference between points a and c ? (d) Plot the electric potential as a function of position along the loop $a \rightarrow b \rightarrow c \rightarrow a$.



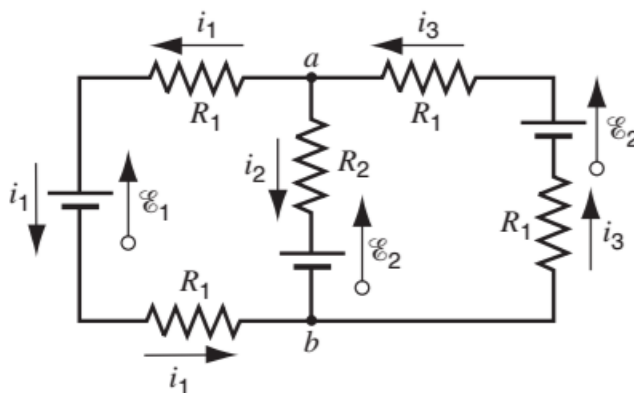
2. (RHK Sample 31-3+4) (a) Find the currents in the circuit below, if $\mathcal{E}_1 = 2, \mathcal{E}_2 = 6, R_1 = 2, R_2 = 4$.
 (b) What is the potential difference between points a and b ?



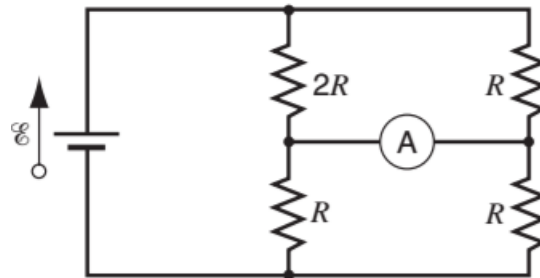
3. (RHK Exercise 31-11) What current, in terms of \mathcal{E} and R , does the ammeter A measure in the circuit below? (Assume that A has zero resistance)



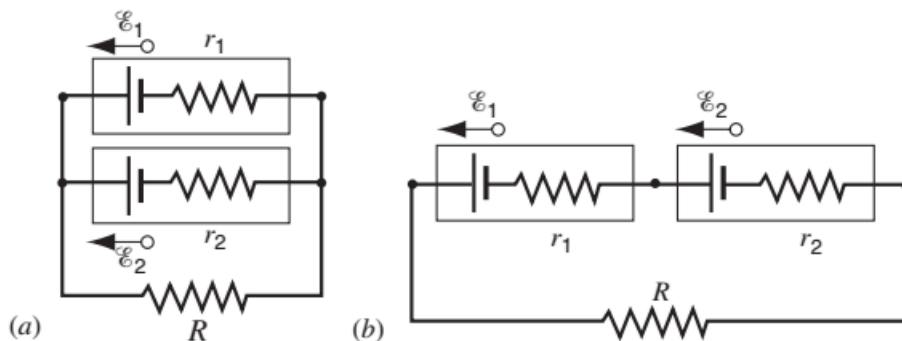4. (RHK Exercise 31-12) You are given two batteries of emf values \mathcal{E}_1 and \mathcal{E}_2 and internal resistances r_1 and r_2 . They may be connected either in (a) parallel or (b) series and are used to establish a current in a resistor R as shown in the diagrams below. Derive expressions for the current in R for both configurations. (c) If $r_1 = r_2 = r$, for what r is the power dissipated by R maximized in each configuration? (d) What is the maximum power dissipation in either case?




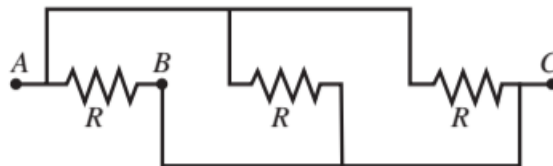5. (RHK Exercise 31-18) Find the equivalent resistance between points (a) A and B , (b) B and C , (c) B and C .



6. (RHK Exercise 31-20) A 120 V power line is protected by a 15 A fuse. What is the maximum number of 500 W lamps that can be simultaneously operated in parallel on this line?

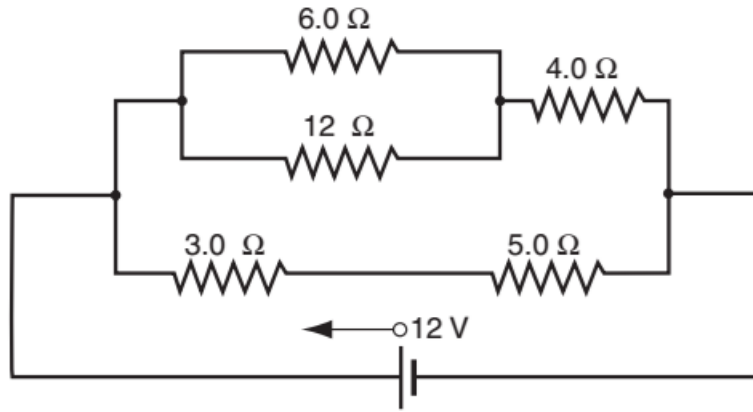7. (RHK Exercise 31-19) A circuit containing five resistors connected to a 12 V battery is shown below. Find the potential difference across the 5.0 Ω resistor.



8. (RHK Exercise 31-24) In the circuit below, \mathcal{E} , R_1 , and R_2 have constant values, but R can be varied. Find an expression for R that results in the maximum power dissipation in the whole circuit.

